


Rosette Strain Gages & Wheatstone Bridges



Jessica Goetz

Strain Gages

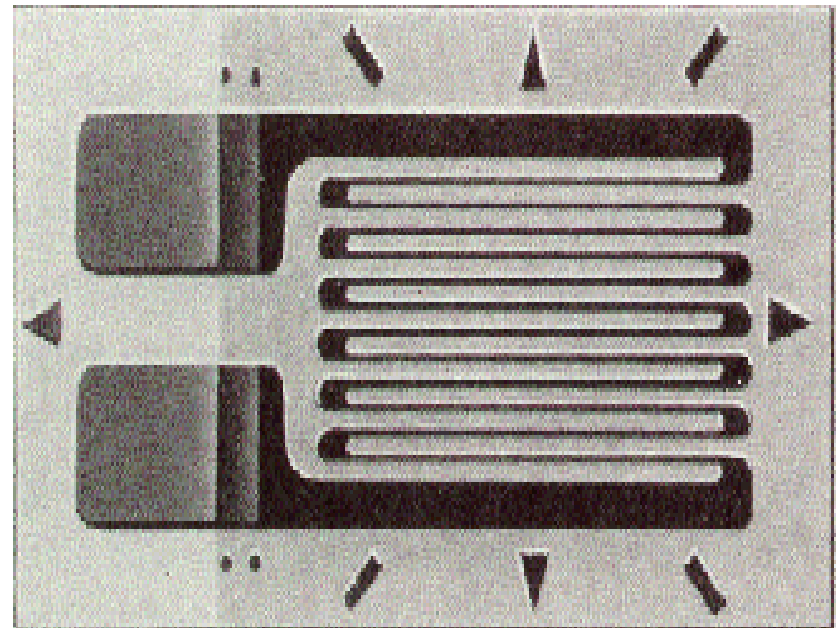- ⌘ The most common type of strain gage is an electrical resistance strain gage
- ⌘ It measures strain based on the change in resistance of the wire as the object is strained



Strain Gages




⌘ When a wire is strained, the wire's resistance changes according to changes in the wire's diameter, length and resistivity

$$\text{⌘ } R = \rho^* L/A$$

Wheatstone Bridges

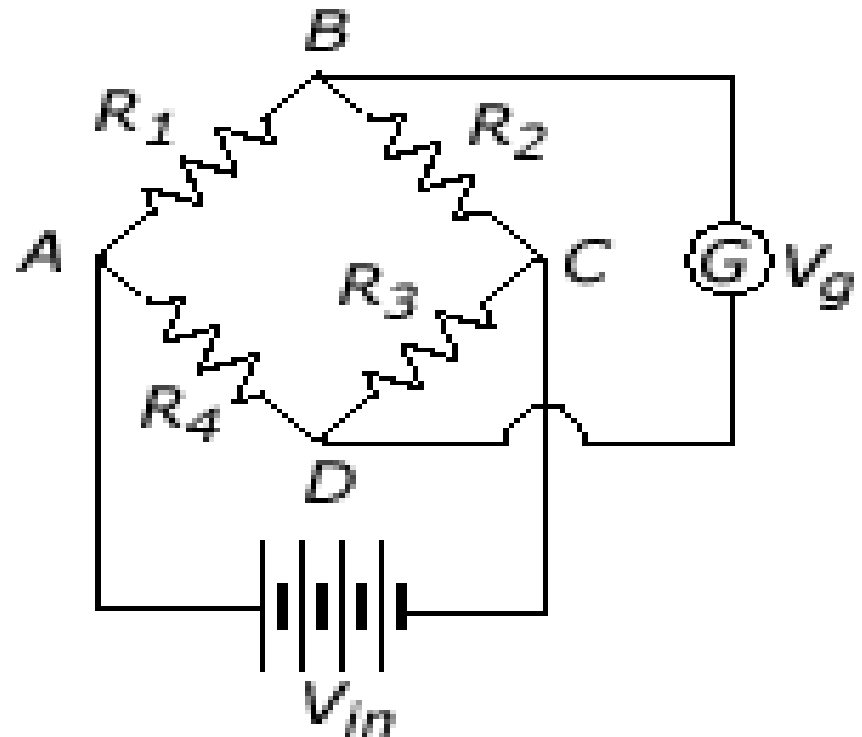- ⌘ The changes in resistance of the strain gages are most easily measured by a Wheatstone bridge
- ⌘ Determines the change in resistance by comparison to known resistances




Wheatstone Bridges


⌘ Bridges are balanced when the voltage read across the middle of the circuit is zero

⌘ $R_1/R_2 = R_4/R_3$

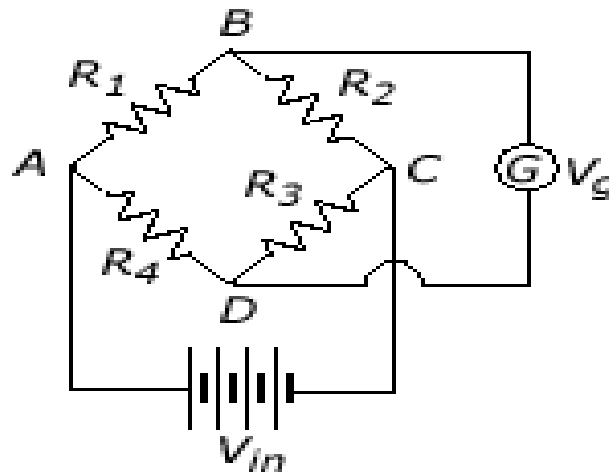⌘ V_g will read zero and the bridge will be balanced



Wheatstone Bridge

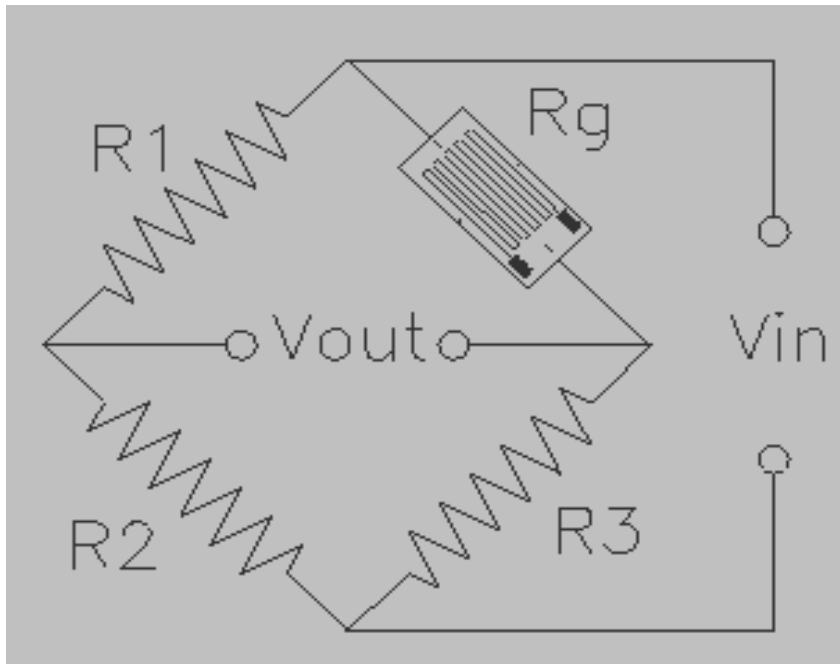


- ⌘ A Wheatstone bridge is four resistors, a constant input voltage and a voltage gage
- ⌘ Three of the four resistances are known and the fourth can be determined by balancing the bridge

Wheatstone Bridges

- ⌘ Resistors in a Wheatstone bridge can be of variable resistance, such as a strain gage
- ⌘ If the resistance in the strain gage changes, a voltage will develop across the Wheatstone bridge
- ⌘ The measured voltage can be used to calculate the change in resistance in the strain gage and therefore the strain
- ⌘ $V_g + \Delta V_g = \frac{(R_1 + \Delta R_1)(R_3 + \Delta R_3) - (R_2 + \Delta R_2)(R_4 + \Delta R_4)}{(R_1 + \Delta R_1 + R_2 + \Delta R_2)(R_4 + \Delta R_4 + R_3 + \Delta R_3)} * V_{in}$
- ⌘

Rosette Strain Gages

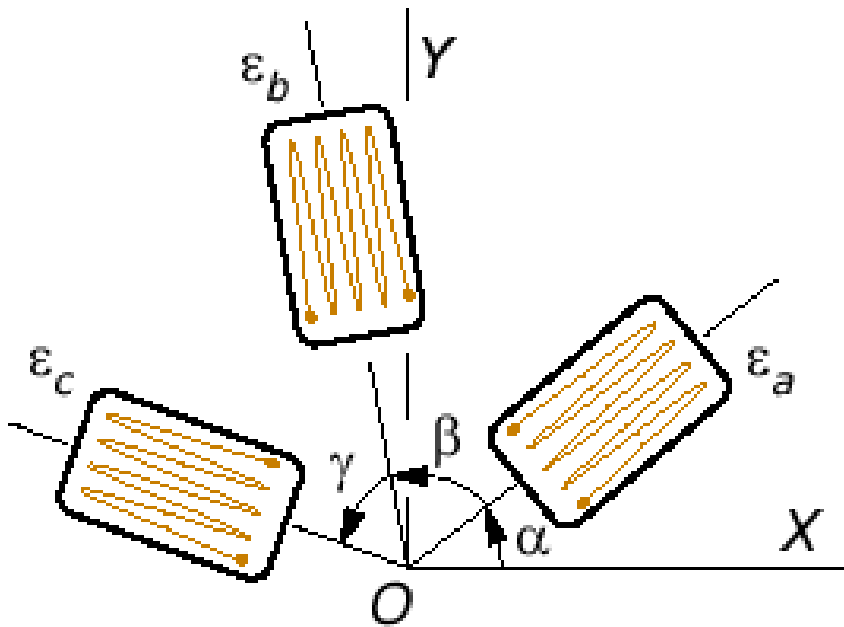

- ⌘ A strain gage only measures strain in one direction
- ⌘ To get principal strains, it is necessary to use a strain rosette
- ⌘ A strain rosette is a cluster of 3 strain gages oriented at different angles

Rosette Strain Gauges

⌘ The set of equations relating rosette measured strains to principal strains are:

$$\boxed{\times} \epsilon_a = \epsilon_x \cos^2 \theta_a + \epsilon_y \sin^2 \theta_a + \gamma_{xy} \sin \theta_a \cos \theta_a$$




$$\boxed{\times} \epsilon_b = \epsilon_x \cos^2 \theta_b + \epsilon_y \sin^2 \theta_b + \gamma_{xy} \sin \theta_b \cos \theta_b$$

$$\boxed{\times} \epsilon_c = \epsilon_x \cos^2 \theta_c + \epsilon_y \sin^2 \theta_c + \gamma_{xy} \sin \theta_c \cos \theta_c$$

$\boxed{\times} \epsilon_a, \epsilon_b, \epsilon_c$ are the strains measured by the individual strain gages in the rosette

Uses of Strain Gages

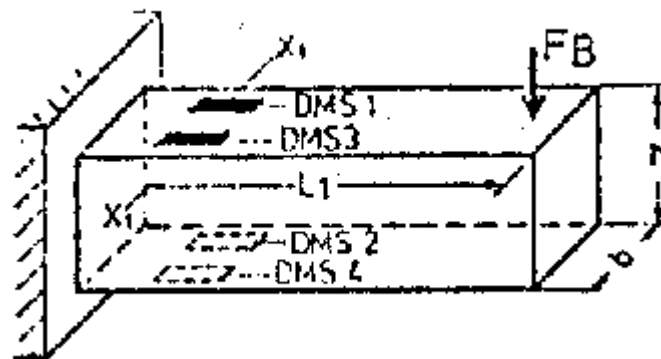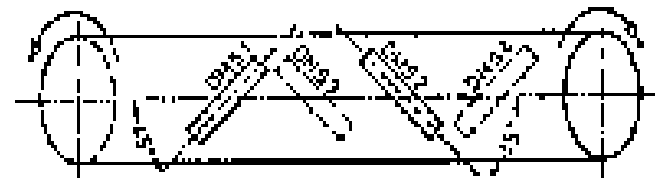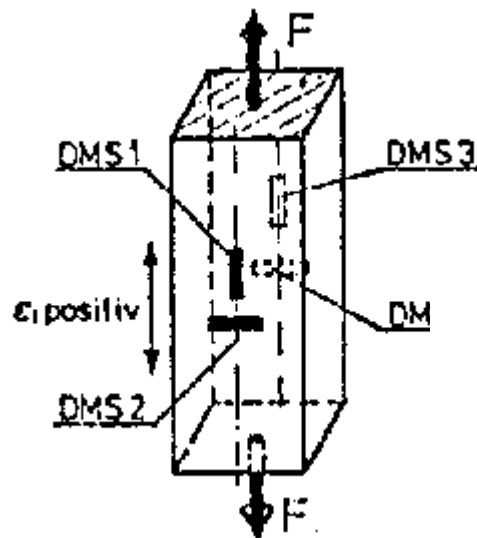⌘ Strain gages attached to Wheatstone bridges can be used for measurement of tension, bending, and torsion



Uses of Strain Gages



- ⌘ In biomedical applications, strain gages can be used for determining forces in bones
- ⌘ Slightly modified strain gages can be used for muscle contraction and blood pressure measurement

References



- ⌘ "AC and DC Bridges." Retrieved August 29, 2002 from the World Wide Web:
<http://www.davv.ac.in.lectures/elex6/Bridge.htm>.
- ⌘ Efun da. "Rosette Strain Gauge." Retrieved August 29, 2002 from the World Wide Web:
http://www.efunda.com/formulae/solid_mechanics/mat_mechanics/st_rain_gage/rosette.cfm.
- ⌘ Hibbler R.C. *Mechanics of Materials Fourth Ed.* New Jersey: Prentice Hall, 2000.
- ⌘ Hoffmann, Karl. "Applying the Wheatstone Bridge." Retrieved September 8, 2002 from the World Wide Web:
<http://www.gisc.co.kr/weigh/wheatstn.html>.

References



- ⌘ Scott, Richard H. "Strain Gauges." Retrieved September 8, 2002 from the World Wide Web: <http://www.dur.ac.un.richard.scott/gauges.html>.
- ⌘ Sharp, James H. "Measurements of Strain." Retrieved September 8, 2002 from the World Wide Web: <http://www.mech.gla.ac.uk/~sharpj/lectures/ids/notes/strain.pdf>.
- ⌘ Webster, John G. Ed. *Medical Instrumentation: Application and Design Third Ed.* New York: John Wiley & Sons Inc. 1998.
- ⌘ "Wheatstone Bridge Circuit." Retrieved August 29, 2002 from the World Wide Web: http://civil.colorado.edu/couseware/struct_labs/wheatstone.html.